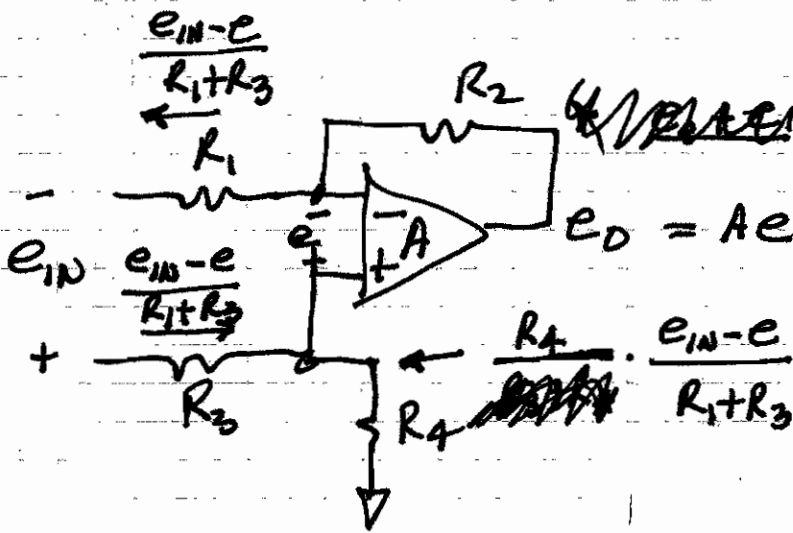


Differential  
Input  
Impedance  
with  
Finite  
Gain = A



$$e_o = \frac{R_4}{R_1 + R_3} \cdot \frac{e_{IN} - e}{R_1 + R_3} - e + \frac{e_{IN} - e}{R_1 + R_3} R_2$$

$$e_o = \frac{R_2 + R_4}{R_1 + R_3} \cdot e_{IN} - e \left[ 1 + \frac{R_4 + R_2}{R_1 + R_3} \right]$$

$$e_o = \frac{R_2 + R_4}{R_1 + R_3} \cdot e_{IN} - \frac{e_o}{A} \left[ \frac{R_1 + R_2 + R_3 + R_4}{R_1 + R_3} \right]$$

$$e_o \left[ 1 + \frac{R_1 + R_2 + R_3 + R_4}{A(R_1 + R_3)} \right] = \frac{R_2 + R_4}{R_1 + R_3} e_{IN}$$

$$e_o \left[ \frac{A(R_1 + R_3) + R_1 + R_2 + R_3 + R_4}{A} \right] = (R_2 + R_4) e_{IN}$$

$$\frac{e_o}{e_{IN}} = \frac{A(R_2 + R_4)}{A(R_1 + R_3) + R_1 + R_2 + R_3 + R_4}$$

(2)

$$Z_{IN} = \frac{e_{IN} - e}{R_1 + R_3} = \frac{e_{IN} - \frac{e_0}{A}}{R_1 + R_3}$$

$$Z_{IN} = \frac{e_{IN}}{(e_{IN} - e)} (R_1 + R_3)$$

$$Z_{IN} = \frac{e_{IN}}{(e_{IN} - \frac{e_0}{A})} (R_1 + R_3)$$

$$\frac{e_0}{A} = \frac{R_2 + R_4}{A(R_1 + R_3) + R_1 + R_2 + R_3 + R_4} e_{IN}$$

$$Z_{IN} = \frac{e_{IN} (R_1 + R_3)}{e_{IN} - \frac{(R_2 + R_4)}{A(R_1 + R_3) + R_1 + R_2 + R_3 + R_4} e_{IN}}$$

$$Z_{IN} = \frac{[A(R_1 + R_3) + R_1 + R_2 + R_3 + R_4] \cdot (R_1 + R_3)}{A(R_1 + R_3) + R_1 + R_2 + R_3 + R_4 - \frac{R_2 + R_4}{A} - \frac{R_2 + R_4}{A}}$$

$$Z_{IN} = \frac{A(R_1 + R_3) + R_1 + R_2 + R_3 + R_4}{A + 1}$$